

OR GATE DATAFLOW MODEL

VHD code

entity OR_GATE is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end OR_GATE;


architecture DATAFLOW of OR_GATE is

begin

C<= A OR B;

end DATAFLOW;

SCHEMEATIC DIAGRAM

 

TBW Code

entity or_gate_flow is

-- Port ();

end or_gate_flow;

architecture DATAFLOW of or_gate_flow is

component OR_GATE is

Port(A: in STD_LOGIC;

B: in STD_LOGIC;

C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

```

begin

UUT:OR_GATE port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

wait for 100ns;

A1<='1';B1<='1';


wait;

end process;

end DATAFLOW;

```

TBW Waveform

 

NOT GATE DATAFLOW MODEL

VHD code

```

entity NOT_GATE is

    Port ( A : in STD_LOGIC;

          B : out STD_LOGIC);

end NOT_GATE;

architecture DATAFLOW of NOT_GATE is


begin

B<= NOT A;

end DATAFLOW;

```

SCHEMEATIC DIAGRAM

 

TBW Code

entity not_gate_flow is

-- Port ();

end not_gate_flow;

architecture DATAFLOW of not_gate_flow is

component NOT_GATE is

Port(A: in STD_LOGIC;

B: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC;

begin

UUT:NOT_GATE port map(A=>A1, B=>B1);

Stim_proc:process

begin

wait for 100ns;

A1<='0';

wait for 100ns;


A1<='1';

wait;

end process;

end DATAFLOW;

TBW Waveform

 


NAND GATE DATAFLOW MODEL

VHD code

```
entity NAND_GATE is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          C : out STD_LOGIC);
end NAND_GATE;

architecture DATAFLOW of NAND_GATE is
begin
    c<=NOT( A AND B);
end DATAFLOW;
```

SCHEMEATIC DIAGRAM

 

TBW Code

```
entity nand_gate_flow is
-- Port ();
end nand_gate_flow;

architecture DATAFLOW of nand_gate_flow is
component NAND_GATE is
    Port( A: in STD_LOGIC;
```

```

        B: in STD_LOGIC;

        C: out STD_LOGIC);

    end component;

    Signal A1:STD_LOGIC:= '0';

    Signal B1:STD_LOGIC:= '0';

    Signal C1:STD_LOGIC;

begin

    UUT:NAND_GATE port map(A=>A1, B=>B1, C=>C1);

    Stim_proc:process

    begin

        wait for 100ns;

        A1<='0';B1<='0';

        wait for 100ns;

        A1<='0';B1<='1';

        wait for 100ns;

        A1<='1';B1<='0';

        wait for 100ns;

        A1<='1';B1<='1';


        wait;

    end process;

end DATAFLOW;

```

TBW Waveform

 

NOR GATE DATAFLOW MODEL

VHD code

entity NOR_GATE is

```

    Port ( A : in STD_LOGIC;

```

```

    B : in STD_LOGIC;

    C : out STD_LOGIC);

end NOR_GATE;

architecture DATAFLOW of NOR_GATE is


begin

C<= NOT(A OR B);

end DATAFLOW;

```

SCHEMEATIC DIAGRAM

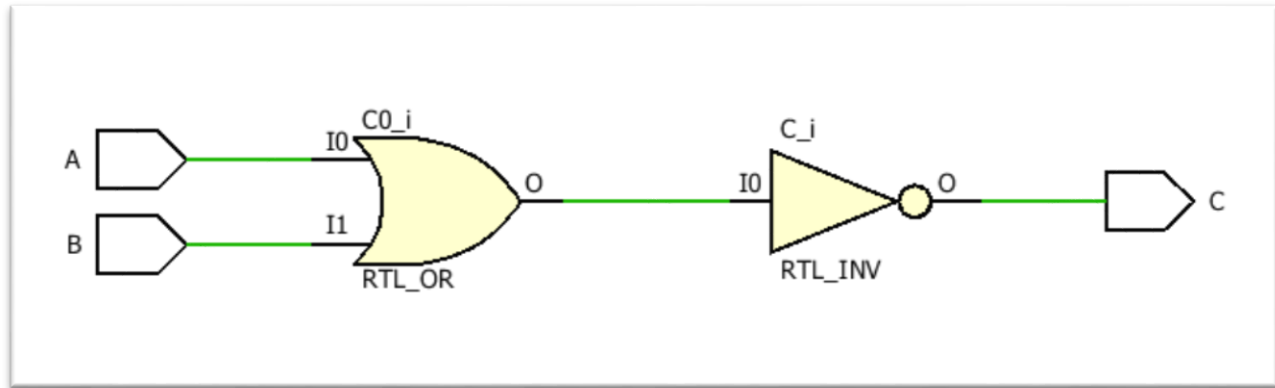

TBW Code

```

entity nor_gate_flow is

-- Port ( );

end nor_gate_flow;

architecture DATAFLOW of nor_gate_flow is

component NOR_GATE is

    Port( A: in STD_LOGIC;

        B: in STD_LOGIC;

        C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

begin

UUT:NOR_GATE port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process

begin

wait for 100ns;

```

```
A1<='0';B1<='0';
```

```
wait for 100ns;
```

```
A1<='0';B1<='1';
```

```
wait for 100ns;
```

```
A1<='1';B1<='0';
```

```
wait for 100ns;
```


```
A1<='1';B1<='1';
```

```
wait;
```

```
end process;
```

```
end DATAFLOW;
```

TBW Waveform

 

AND GATE DATAFLOW MODEL

VHD code

```
entity AND_GATE is
```

```
Port ( A : in STD_LOGIC;
```

```
      B : in STD_LOGIC;
```

```
      C : out STD_LOGIC);
```

```
end AND_GATE;
```


```
architecture DATAFLOW of AND_GATE is
```

```
begin
```

```
C<= A AND B;
```

```
end DATAFLOW;
```

SCHEMEATIC DIAGRAM

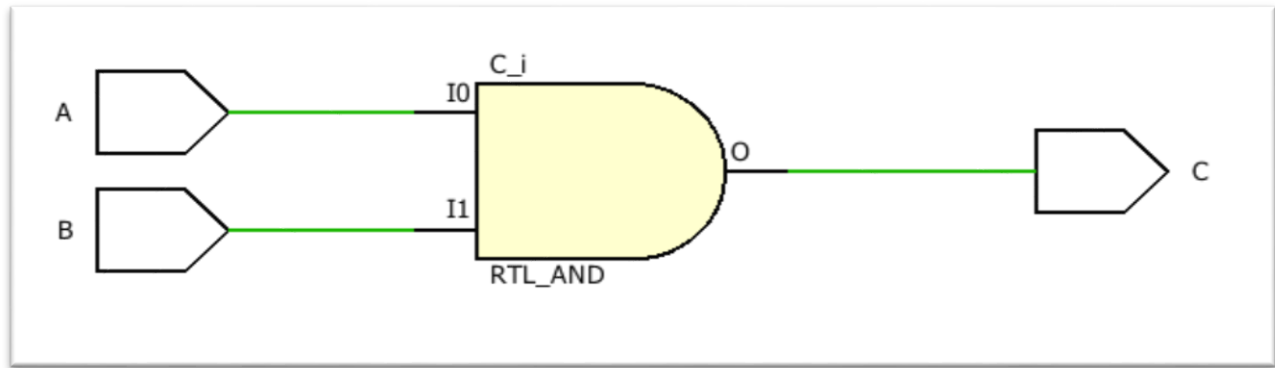

TBW Code

entity and_gate_flow is

```
-- Port ( );
```

```
end and_gate_flow;
```

architecture DATAFLOW of and_gate_flow is

component AND_GATE is

```
Port( A: in STD_LOGIC;
```

```
      B: in STD_LOGIC;
```

```
      C: out STD_LOGIC);
```

```
end component;
```

```
Signal A1:STD_LOGIC:= '0';
```

```
Signal B1:STD_LOGIC:= '0';
```

```
Signal C1:STD_LOGIC;
```

```
begin
```

```
UUT:AND_GATE port map(A=>A1, B=>B1, C=>C1);
```

```
Stim_proc:process
```

```
begin
```

```
wait for 100ns;
```

```
A1<='0';B1<='0';
```

```
wait for 100ns;
```

```
A1<='0';B1<='1';
```

```
wait for 100ns;
```

```
A1<='1';B1<='0';
```

```
wait for 100ns;
```

```
A1<='1';B1<='1';
```


```
wait;
```



```
end process;
```

```
end DATAFLOW;
```

TBW Waveform

 

XOR GATE DATAFLOW MODEL

VHD code

```
entity XOR_GATE is
```

```
  Port ( A : in STD_LOGIC;
```

```
         B : in STD_LOGIC;
```

```
         C : out STD_LOGIC);
```

```
end XOR_GATE;
```


```
architecture DATAFLOW of XOR_GATE is
```

```
begin
```

```
  C<= A XOR B;
```

```
end DATAFLOW;
```

SCHEMEATIC DIAGRAM

 

TBW Code

```
entity xor_gate_flow is
```

```
-- Port ( );
```

```

end xor_gate_flow;

architecture DATAFLOW of xor_gate_flow is

component XOR_GATE is

    Port( A: in STD_LOGIC;

          B: in STD_LOGIC;

          C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

begin

UUT:XOR_GATE port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

wait for 100ns;

A1<='1';B1<='1';


wait;

end process;

end DATAFLOW;

```

TBW Waveform

 

XNOR GATE DATAFLOW MODEL

VHD code

entity XNOR_GATE is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end XNOR_GATE;


architecture DATAFLOW of XNOR_GATE is

begin

C<= A XNOR B;

end DATAFLOW;

SCHEMEATIC DIAGRAM

 

TBW Code

entity xnor_gate_flow is

-- Port ();

end xnor_gate_flow;

architecture DATAFLOW of xnor_gate_flow is

component XNOR_GATE is

Port(A: in STD_LOGIC;

B: in STD_LOGIC;

C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

begin


UUT:XNOR_GATE port map(A=>A1, B=>B1, C=>C1);

```

Stim_proc:process
begin
wait for 100ns;
A1<='0';B1<='0';
wait for 100ns;
A1<='0';B1<='1';
wait for 100ns;
A1<='1';B1<='0';
wait for 100ns;
A1<='1';B1<='1';
wait;
end process;
end DATAFLOW;

```

TBW Waveform

 

AND GATE FORM NAND GATE DATAFLOW MODEL

VHD code

entity NAND_AND is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end NAND_AND;


architecture Behavioral of NAND_AND is

begin

C<= (A NAND B) NAND (A NAND B);

end Behavioral;

SCHEMEATIC DIAGRAM

 

TBW Code

entity nand_and_gate_flow is

-- Port ();

end nand_and_gate_flow;

architecture DATAFLOW of nand_and_gate_flow is

component NAND_AND is

Port(A: in STD_LOGIC;

B: in STD_LOGIC;

C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

begin

UUT:NAND_AND port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process

```

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

wait for 100ns;

A1<='1';B1<='1';


wait;

end process;

end DATAFLOW;

```

TBW Waveform

 

OR GATE FORM NAND GATE DATAFLOW MODEL

VHD code


```

entity NAND_OR is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end NAND_OR;

architecture Behavioral of NAND_OR is
begin
    C<= (A NAND A) NAND (B NAND B);
end Behavioral;

```

SCHEMEATIC DIAGRAM

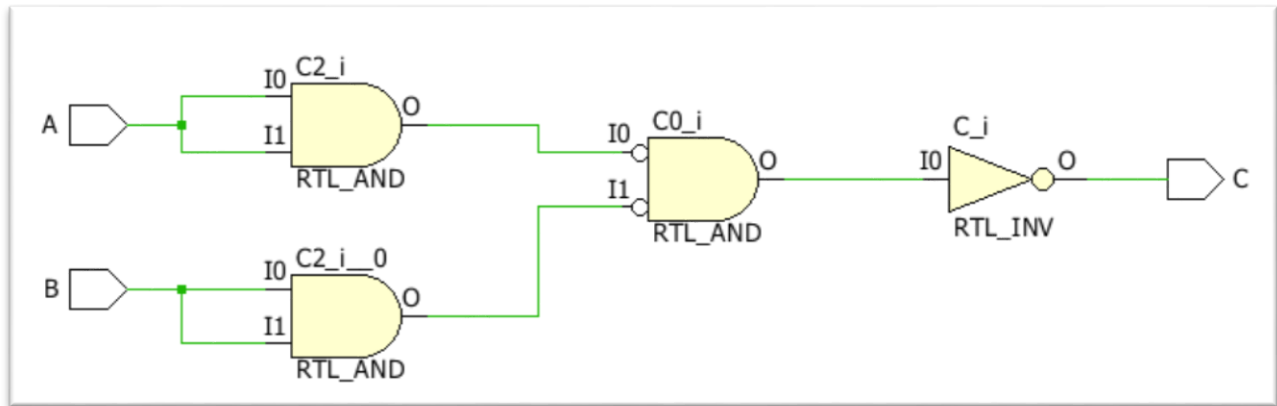

TBW Code

entity nand_or_gate_flow is

-- Port ();

end nand_or_gate_flow;

architecture DATAFLOW of nand_or_gate_flow is

component NAND_OR is

Port(A: in STD_LOGIC;

B: in STD_LOGIC;

C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

begin

UUT:NAND_OR port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

wait for 100ns;


A1<='1';B1<='1';

wait;

```
end process;

end DATAFLOW;
```

TBW Waveform

 


NOT GATE FORM NAND GATE DATAFLOW MODEL

VHD code

```
entity NAND_NOT is
    Port ( A : in STD_LOGIC;
          C : out STD_LOGIC);
end NAND_NOT;

architecture DATAFLOW of NAND_NOT is
begin
    C<= A NAND A;
end DATAFLOW;
```

SCHEMEATIC DIAGRAM

 

TBW Code

```
entity nand_not_gate_flow is
-- Port ();
end nand_not_gate_flow;

architecture DATAFLOW of nand_not_gate_flow is
    component NAND_NOT is
```



```

Port( A: in STD_LOGIC;

      C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

begin

UUT:NAND_NOT port map(A=>A1,C=>C1);

Stim_proc:process

begin

wait for 100ns;

A1<='0';

wait for 100ns;

A1<='1';


wait;

end process;

end DATAFLOW;

```

TBW Waveform

 

XOR GATE FORM NAND GATE DATAFLOW MODEL

VHD code

```

entity NAND_XOR is

Port ( A : in STD_LOGIC;

      B : in STD_LOGIC;

      C : out STD_LOGIC);

end NAND_XOR;

architecture DATAFLOW of NAND_XOR is


begin

C<= ((A NAND A) NAND B) NAND ((B NAND B) NAND A);

```

end DATAFLOW;

SCHEMEATIC DIAGRAM

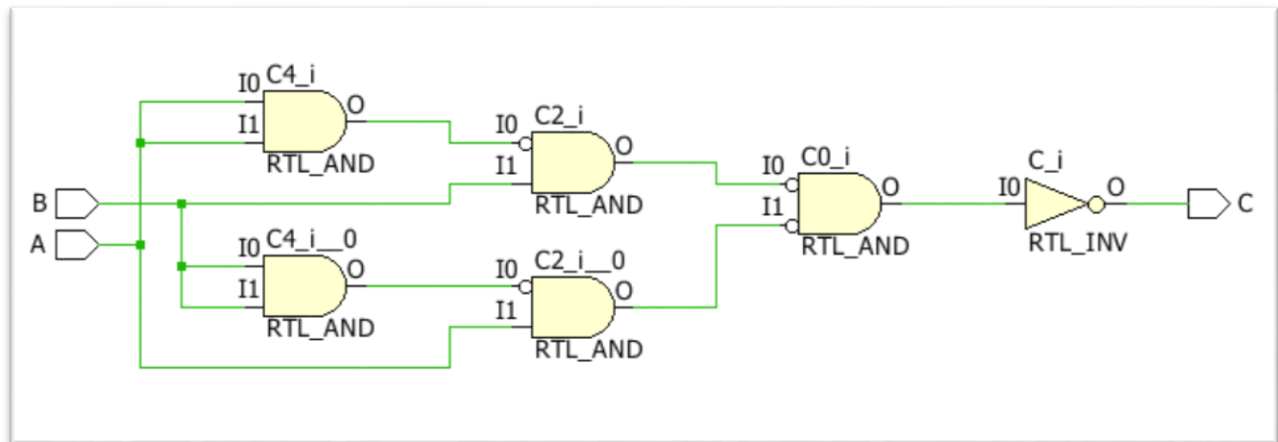

TBW Code

entity nand_xor_gate_flow is

-- Port ();

end nand_xor_gate_flow;

architecture DATAFLOW of nand_xor_gate_flow is

component NAND_XOR is

Port(A: in STD_LOGIC;

B: in STD_LOGIC;

C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

begin

UUT:NAND_XOR port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

```

wait for 100ns;

A1<='1';B1<='1';


wait;

end process;

end DATAFLOW;

```

TBW Waveform

 

XNOR GATE FORM NAND GATE DATAFLOW MODEL

VHD code


```

entity NAND_XNOR is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end NAND_XNOR;

architecture DATAFLOW of NAND_XNOR is
begin
    C<= (A NAND B) NAND ((A NAND A) NAND (B NAND B));
end DATAFLOW;

```

SCHEMEATIC DIAGRAM

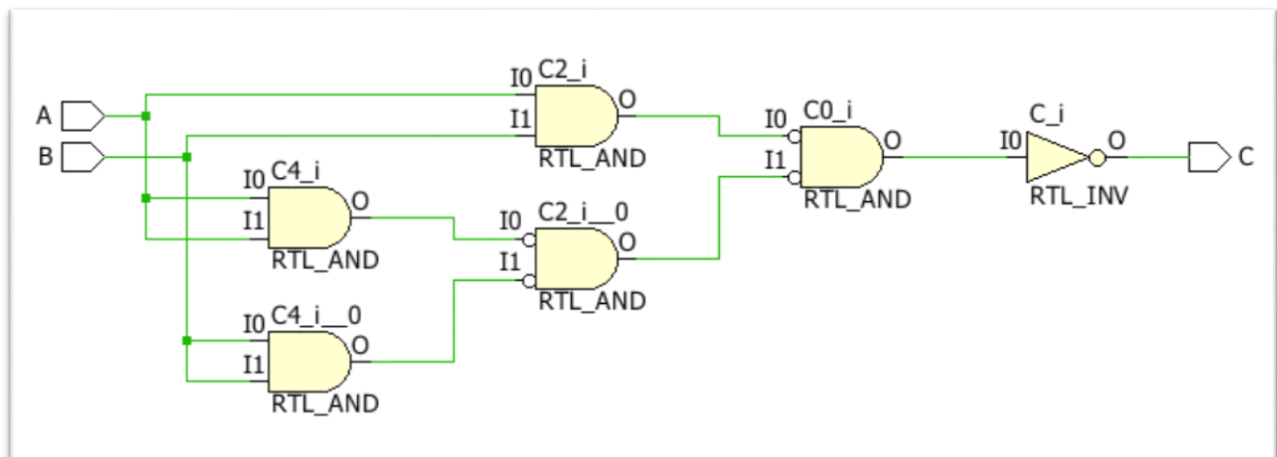

TBW Code

```
entity nand_xnor_gate_flow is
-- Port ( );

end nand_xnor_gate_flow;

architecture DATAFLOW of nand_xnor_gate_flow is

component NAND_XNOR is

    Port( A: in STD_LOGIC;

          B: in STD_LOGIC;

          C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

begin

UUT:NAND_XNOR port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

wait for 100ns;


A1<='1';B1<='1';

wait;

end process;

end DATAFLOW;
```

TBW Waveform

 


NOT GATE FORM NOR GATE DATAFLOW MODEL

VHD code

```
entity NOR_NOT is
    Port ( A : in STD_LOGIC;
           C : out STD_LOGIC);
end NOR_NOT;

architecture DATAFLOW of NOR_NOT is
begin
    C<= A NOR A;
end DATAFLOW;
```

SCHEMEATIC DIAGRAM

 

TBW Code

```
entity nor_not_gate_flow is
-- Port ( );
end nor_not_gate_flow;

architecture DATAFLOW of nor_not_gate_flow is
    component NOR_NOT is
        Port( A: in STD_LOGIC;
              C: out STD_LOGIC);
    end component;

    Signal A1:STD_LOGIC:= '0';
    Signal C1:STD_LOGIC;

begin
    UUT:NOR_NOT port map(A=>A1,C=>C1);

    Stim_proc:process
```

```

begin
wait for 100ns;

A1<='0';

wait for 100ns;

A1<='1';


wait;

end process;

end DATAFLOW;

```

TBW Waveform

 

OR GATE FORM NOR GATE DATAFLOW MODEL

VHD code


```

entity NOR_OR is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          C : out STD_LOGIC);
end NOR_OR;

architecture DATAFLOW of NOR_OR is
begin
    C<= (A NOR B) NOR (A NOR B);
end DATAFLOW;

```

SCHEMEATIC DIAGRAM

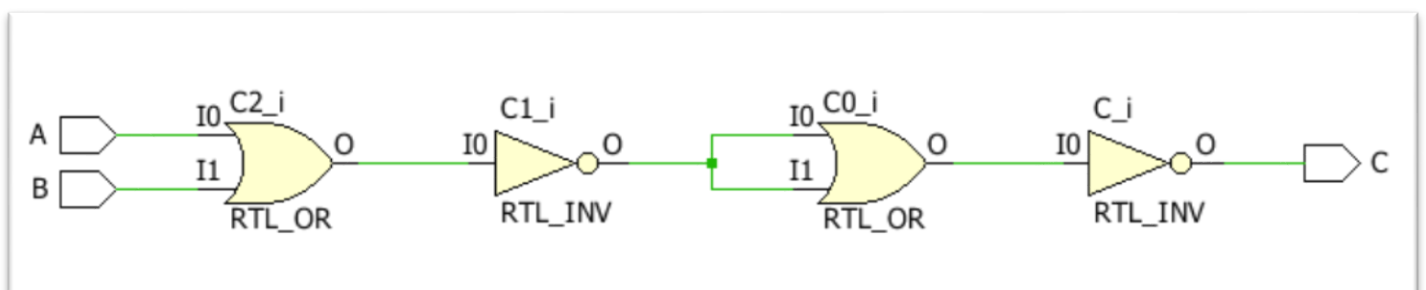

TBW Code

```
entity nor_or_gate_flow is
-- Port ( );

end nor_or_gate_flow;

architecture DATAFLOW of nor_or_gate_flow is

component NOR_OR is

    Port( A: in STD_LOGIC;

          B: in STD_LOGIC;

          C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

begin

UUT:NOR_OR port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

wait for 100ns;


A1<='1';B1<='1';

wait;

end process;

end DATAFLOW;
```

TBW Waveform

 

AND GATE FORM NOR GATE DATAFLOW MODEL

VHD code

entity NOR_AND is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end NOR_AND;


architecture DATAFLOW of NOR_AND is

begin

C<= (A NOR A) NOR (B NOR B);

end DATAFLOW;

SCHEMEATIC DIAGRAM

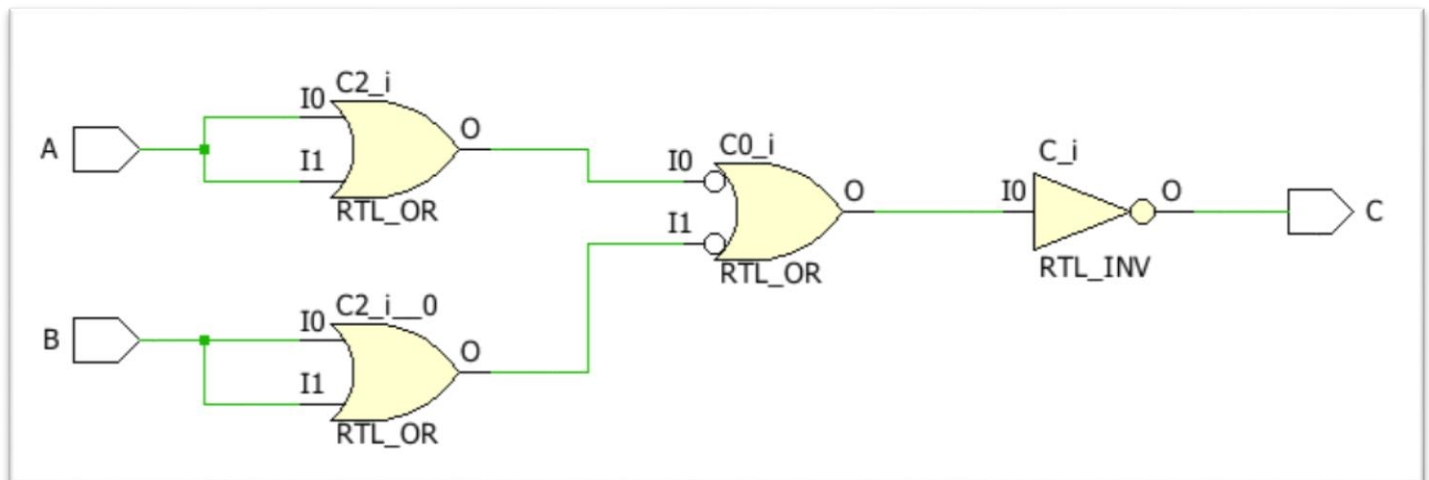

TBW Code

entity nor_and_gate_flow is

-- Port ();

end nor_and_gate_flow;

architecture DATAFLOW of nor_and_gate_flow is

component NOR_AND is

Port(A: in STD_LOGIC;

B: in STD_LOGIC;

C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';


```

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

begin

UUT:NOR_AND port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

wait for 100ns;

A1<='1';B1<='1';


wait;

end process;

end DATAFLOW;

```

TBW Waveform

 

XOR GATE FORM NOR GATE DATAFLOW MODEL

VHD code

```

entity NOR_XOR is

Port ( A : in STD_LOGIC;

      B : in STD_LOGIC;

      C : out STD_LOGIC);

end NOR_XOR;

architecture DATAFLOW of NOR_XOR is


begin

C<= (A NOR B) NOR ( (A NOR A) NOR (B NOR B) );

```

end DATAFLOW;

SCHEMEATIC DIAGRAM

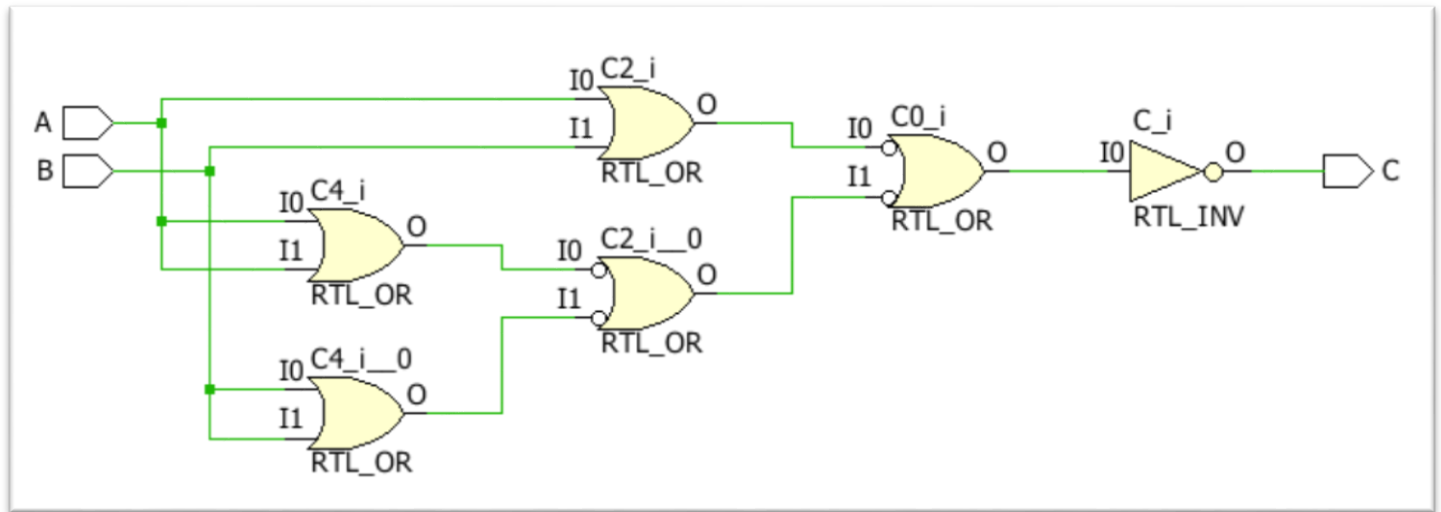

TBW Code

entity nor_xor_gate_flow is

-- Port ();

end nor_xor_gate_flow;

architecture DATAFLOW of nor_xor_gate_flow is

component NOR_XOR is

Port(A: in STD_LOGIC;

B: in STD_LOGIC;

C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

begin

UUT:NOR_XOR port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

```

A1<='1';B1<='0';

wait for 100ns;

A1<='1';B1<='1';


wait;

end process;

end DATAFLOW;

```

TBW Waveform

 

XNOR GATE FORM NOR GATE DATAFLOW MODEL

VHD code


```

entity NOR_XNOR is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          C : out STD_LOGIC);
end NOR_XNOR;

architecture DATAFLOW of NOR_XNOR is
begin
    C<= (A NOR (A NOR B)) NOR (B NOR (A NOR B));
end DATAFLOW;

```

SCHEMEATIC DIAGRAM

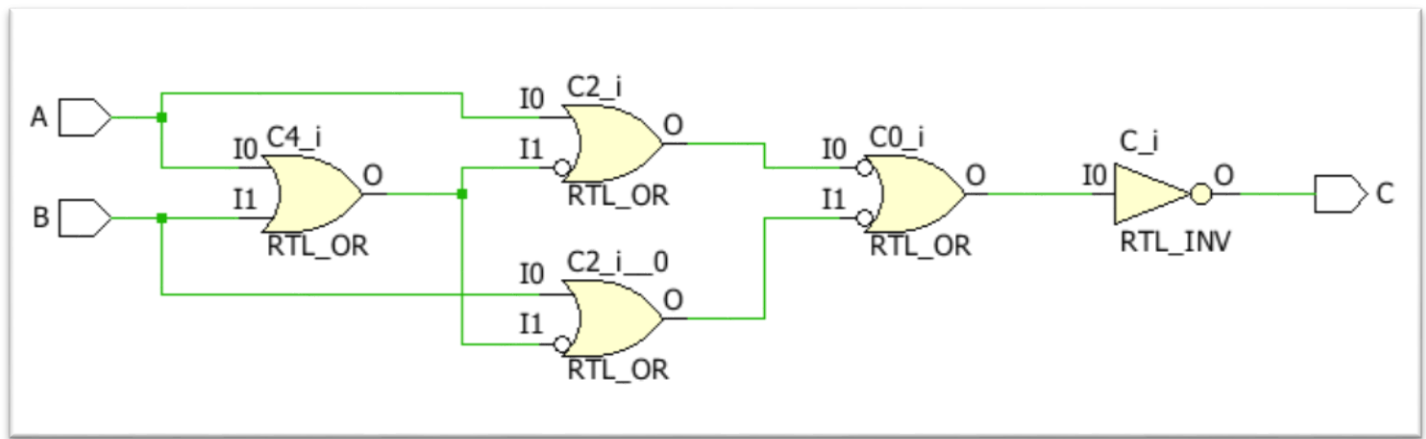

TBW Code

entity nor_xnor_gate_flow is

-- Port ();

end nor_xnor_gate_flow;

architecture DATAFLOW of nor_xnor_gate_flow is

component NOR_XNOR is

Port(A: in STD_LOGIC;

B: in STD_LOGIC;

C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

begin

UUT:NOR_XNOR port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;


A1<='1';B1<='0';

wait for 100ns;

A1<='1';B1<='1';

```
wait;  
end process;  
end DATAFLOW;
```

TBW Waveform

 

OR GATE BEHAVIORAL MODEL

VHD code

entity OR_GATE is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end OR_GATE;

architecture Behavioral of OR_GATE is

begin

process(A,B)

begin

if(A ='1' or B='1') then

C<='1';

else


C<='0';

end if;

end process;

end Behavioral;

SCHEMEATIC DIAGRAM

 

TBW Code

entity or_gate_flow is

-- Port ();

end or_gate_flow;

architecture Behavioral of or_gate_flow is

component OR_GATE is

```

Port( A: in STD_LOGIC;

      B: in STD_LOGIC;

      C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC;

begin

UUT:OR_GATE port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

wait for 100ns;

A1<='1';B1<='1';


wait;

end process;

end Behavioral;

```

TBW Waveform

 

NOT GATE BEHAVIORAL MODEL

VHD code

entity NOT_GATE is

```


Port ( A : in STD_LOGIC;
      B : out STD_LOGIC);

end NOT_GATE;

architecture Behavioral of NOT_GATE is
begin
process(A)
begin
if(A ='0') then
    B<='1';
else
    B<='0';
end if;
end process;
end Behavioral;

```

SCHEMEATIC DIAGRAM

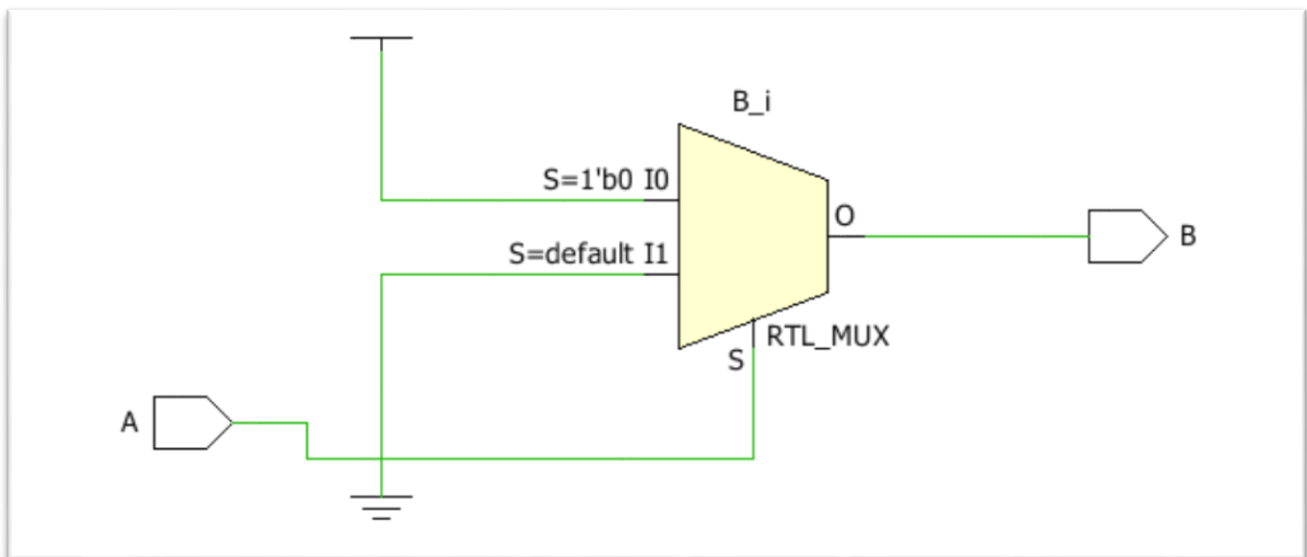

TBW Code

```

entity not_gate_flow is
-- Port ( );
end not_gate_flow;

architecture Behavioral of not_gate_flow is
component NOT_GATE is
    Port( A: in STD_LOGIC;

```



```

        B: out STD_LOGIC);

    end component;

    Signal A1:STD_LOGIC:=0';

    Signal B1:STD_LOGIC;

begin

    UUT:NOT_GATE port map(A=>A1, B=>B1);

    Stim_proc:process

    begin

        wait for 100ns;

        A1<='0';

        wait for 100ns;

        A1<='1';


        wait;

    end process;

end Behavioral;

```

TBW Waveform

 

NAND GATE BEHAVIORAL MODEL

VHD code

```

entity NAND_GATE is

    Port ( A : in STD_LOGIC;

          B : in STD_LOGIC;

          C : out STD_LOGIC);

end NAND_GATE;

architecture Behavioral of NAND_GATE is

begin

    process(A,B)

    begin

```

```
if(A ='1' and B='1') then
```

```
    C<='0';
```

```
else
```


```
    C<='1';
```

```
end if;
```

```
end process;
```

```
end Behavioral;
```

SCHEMEATIC DIAGRAM

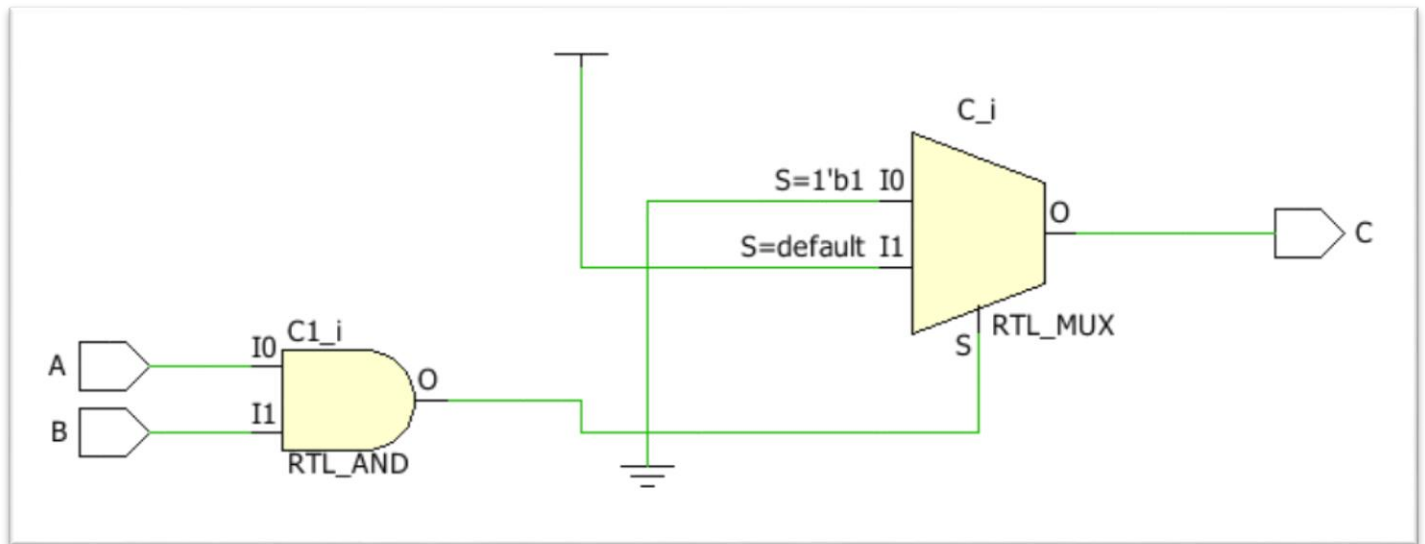

TBW Code

```
entity nand_gate_flow is
```

```
-- Port ( );
```

```
end nand_gate_flow;
```

```
architecture Behavioral of nand_gate_flow is
```

```
component NAND_GATE is
```

```
    Port( A: in STD_LOGIC;
```

```
          B: in STD_LOGIC;
```

```
          C: out STD_LOGIC);
```

```
end component;
```

```
Signal A1:STD_LOGIC:= '0';
```

```
Signal B1:STD_LOGIC:= '0';
```

```
Signal C1:STD_LOGIC;
```

```
begin
```

```
UUT:NAND_GATE port map(A=>A1, B=>B1, C=>C1);
```

```

Stim_proc:process

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

wait for 100ns;

A1<='1';B1<='1';


wait;

end process;

end Behavioral;

```

TBW Waveform

 

NOR GATE BEHAVIORAL MODEL

VHD code

```

entity NOR_GATE is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end NOR_GATE;

architecture Behavioral of NOR_GATE is
begin
    process(A,B)
    begin
        if(A ='0' and B='0') then

```

```

C<='1';

else

C<='0';


end if;

end process;

end Behavioral;

```

SCHEMEATIC DIAGRAM

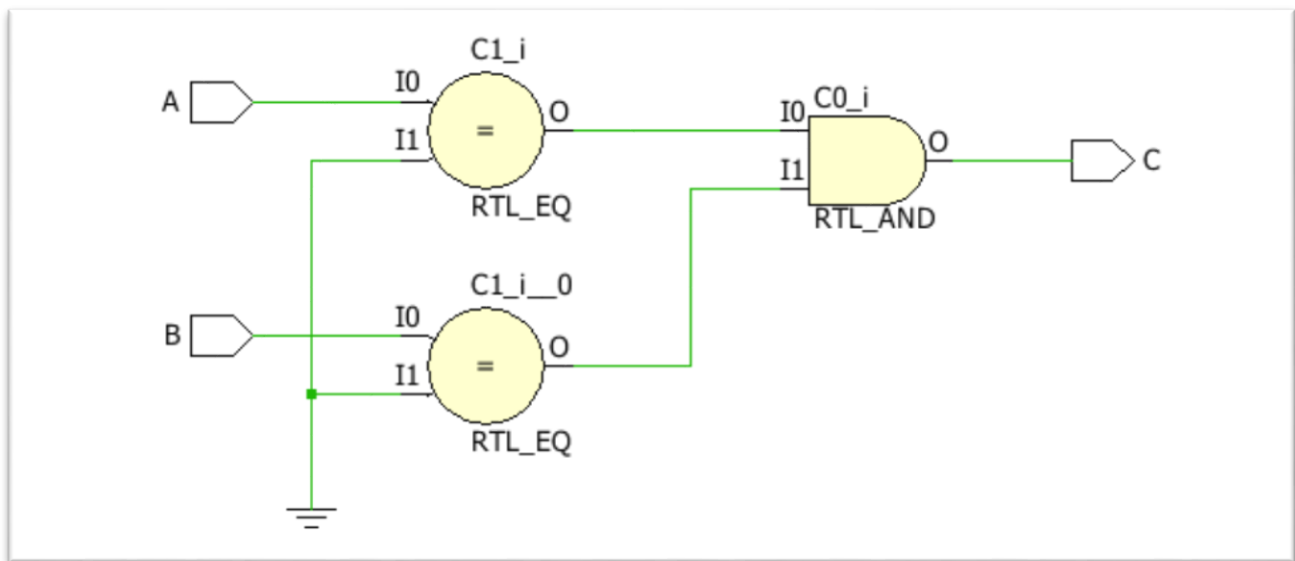

TBW Code

```

entity nor_gate_flow is
-- Port ( );
end nor_gate_flow;

architecture Behavioral of nor_gate_flow is

component NOR_GATE is
    Port( A: in STD_LOGIC;
          B: in STD_LOGIC;
          C: out STD_LOGIC);
end component;

Signal A1:STD_LOGIC:= '0';
Signal B1:STD_LOGIC:= '0';
Signal C1:STD_LOGIC;

begin

UUT:NOR_GATE port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process

```

```

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

wait for 100ns;

A1<='1';B1<='1';


wait;

end process;

end Behavioral;

```

TBW Waveform

 

AND GATE BEHAVIORAL MODEL

VHD code

```

entity AND_GATE is

    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);

end AND_GATE;

architecture Behavioral of AND_GATE is

begin

process(A,B)

begin

if(A ='0' or B='0') then

    C<='0';


```

```


else
    C<='1';
end if;

end process;

end Behavioral;

```

SCHEMEATIC DIAGRAM

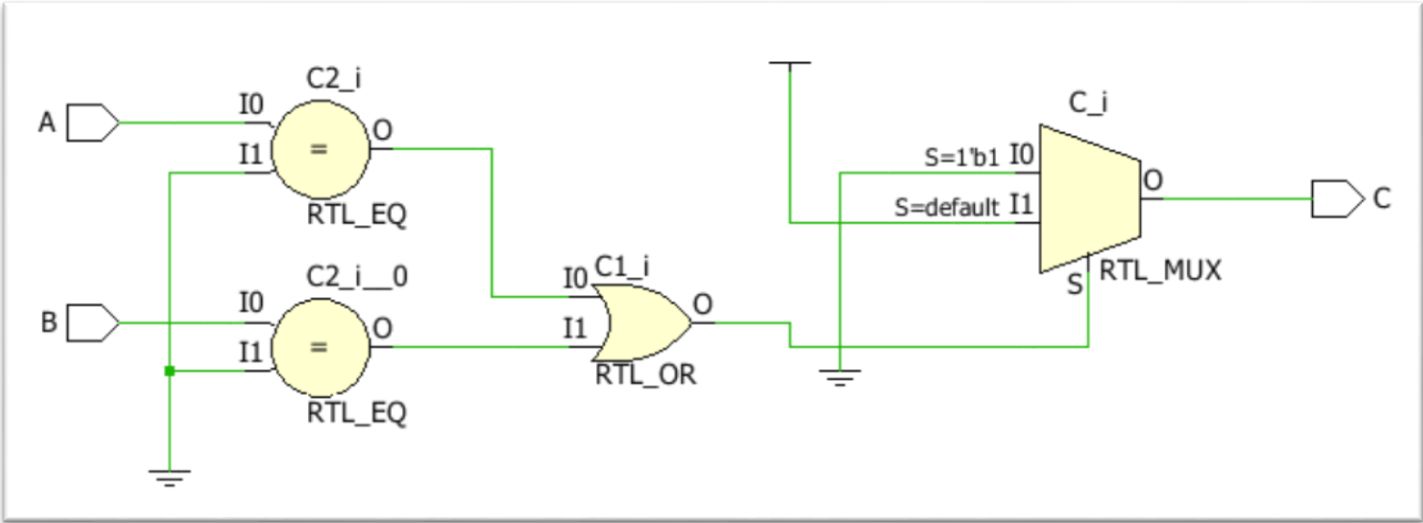

TBW Code

```

entity and_gate_flow is
-- Port ();
end and_gate_flow;

architecture Behavioral of and_gate_flow is
component AND_GATE is
    Port( A: in STD_LOGIC;
          B: in STD_LOGIC;
          C: out STD_LOGIC);
end component;

Signal A1:STD_LOGIC:=0';
Signal B1:STD_LOGIC:=0';
Signal C1:STD_LOGIC;

begin

UUT:AND_GATE port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process
begin
wait for 100ns;

```

```
A1<='0';B1<='0';
```

```
wait for 100ns;
```

```
A1<='0';B1<='1';
```

```
wait for 100ns;
```

```
A1<='1';B1<='0';
```

```
wait for 100ns;
```


```
A1<='1';B1<='1';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

TBW Waveform

 

XOR GATE BEHAVIORAL MODEL

VHD code

```
entity XOR_GATE is
```

```
Port ( A : in STD_LOGIC;
```

```
       B : in STD_LOGIC;
```

```
       C : out STD_LOGIC);
```

```
end XOR_GATE;
```

```
architecture Behavioral of XOR_GATE is
```

```
begin
```

```
process(A,B)
```

```
begin
```

```
if(A = B) then
```

```
    C<='0';
```

```
else
```

```
    C<='1';
```

```
end if;
```


```

end process;

end Behavioral;

```

SCHEMEATIC DIAGRAM

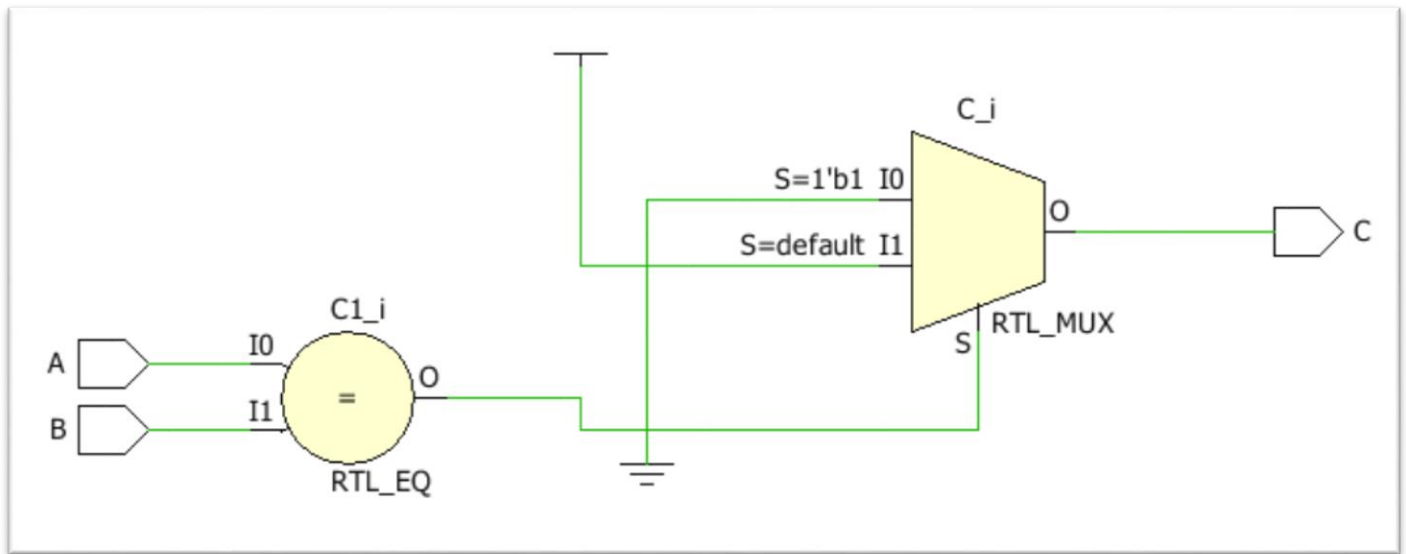

TBW Code

```

entity nor_gate_flow is

```

```

-- Port ( );

```

```

end nor_gate_flow;

```

```

architecture Behavioral of nor_gate_flow is

```

```

component XOR_GATE is

```

```

    Port( A: in STD_LOGIC;

```

```

         B: in STD_LOGIC;

```

```

         C: out STD_LOGIC);

```

```

end component;

```

```

Signal A1:STD_LOGIC:= '0';

```

```

Signal B1:STD_LOGIC:= '0';

```

```

Signal C1:STD_LOGIC;

```

```

begin

```

```

    UUT:XOR_GATE port map(A=>A1, B=>B1, C=>C1);

```

```

    Stim_proc:process

```

```

    begin

```

```

        wait for 100ns;

```

```

        A1<='0';B1<='0';

```



```

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

wait for 100ns;

A1<='1';B1<='1';


wait;

end process;

end Behavioral;

```

TBW Waveform

 

XNOR GATE BEHAVIORAL MODEL

VHD code


```

entity XNOR_GATE is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : out STD_LOGIC);
end XNOR_GATE;

architecture Behavioralof XNOR_GATE is
begin
    process(A,B)
    begin
        if(A = B) then
            C<='1';
        else
            C<='0';
        end if;
    end process;
end Behavioral;

```

SCHEMEATIC DIAGRAM

 

TBW Code

```
entity xnor_gate_flow is
-- Port ( );
end xnor_gate_flow;

architecture Behavioral of xnor_gate_flow is
component XNOR_GATE is
    Port( A: in STD_LOGIC;
          B: in STD_LOGIC;
          C: out STD_LOGIC);
end component;

Signal A1:STD_LOGIC:= '0';
Signal B1:STD_LOGIC:= '0';
Signal C1:STD_LOGIC;

begin

UUT:XNOR_GATE port map(A=>A1, B=>B1, C=>C1);

Stim_proc:process
begin
    wait for 100ns;

    A1<='0';B1<='0';

    wait for 100ns;


    A1<='0';B1<='1';

    wait for 100ns;

    A1<='1';B1<='0';
```

```
wait for 100ns;  
A1<='1';B1<='1';  
  
wait;  
  
end process;  
  
end Behavioral;
```

TBW Waveform

 

HALF ADDER DATAFLOW MODEL

VHD code

entity HALF_ADDER is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

S : out STD_LOGIC;

C : out STD_LOGIC);

end HALF_ADDER;

architecture DATAFLOW of HALF_ADDER is


begin

S<= A XOR B;

C<= A AND B;

end DATAFLOW;

SCHEMEATIC DIAGRAM

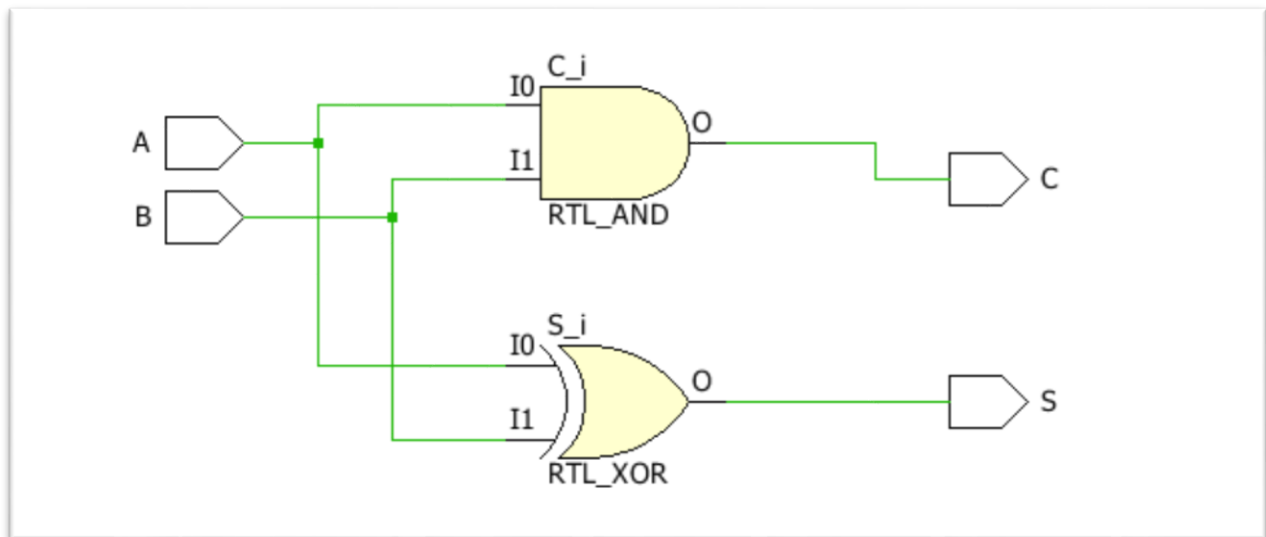

TBW Code

entity half_adder_gate_flow is

-- Port ();

end half_adder_gate_flow;

architecture DATAFLOW of half_adder_gate_flow is

component HALF_ADDER is

Port(A: in STD_LOGIC;

B: in STD_LOGIC;

S: out STD_LOGIC;

```

        C: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal S1:STD_LOGIC;

Signal C1:STD_LOGIC;

begin

UUT:HALF_ADDER port map(A=>A1, B=>B1, S=>S1, C=>C1);

Stim_proc:process

begin

wait for 100ns;

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

wait for 100ns;

A1<='1';B1<='1';


wait;

end process;

end DATAFLOW;

```

TBW Waveform

 

HALF ADDER BEHAVIORAL MODEL

VHD code

```

entity HALF_ADDER is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;

```

```

S : out STD_LOGIC;

C : out STD_LOGIC);

end HALF_ADDER;

architecture Behavioral of HALF_ADDER is

begin

process(A,B)

begin

if(A = B) then

    S<='0';

else

    S<='1';

end if;

if(A='1' and B='1') then

    C<='1';

else

    C<='0';


end if;

end process;

end Behavioral;

```

SCHEMEATIC DIAGRAM

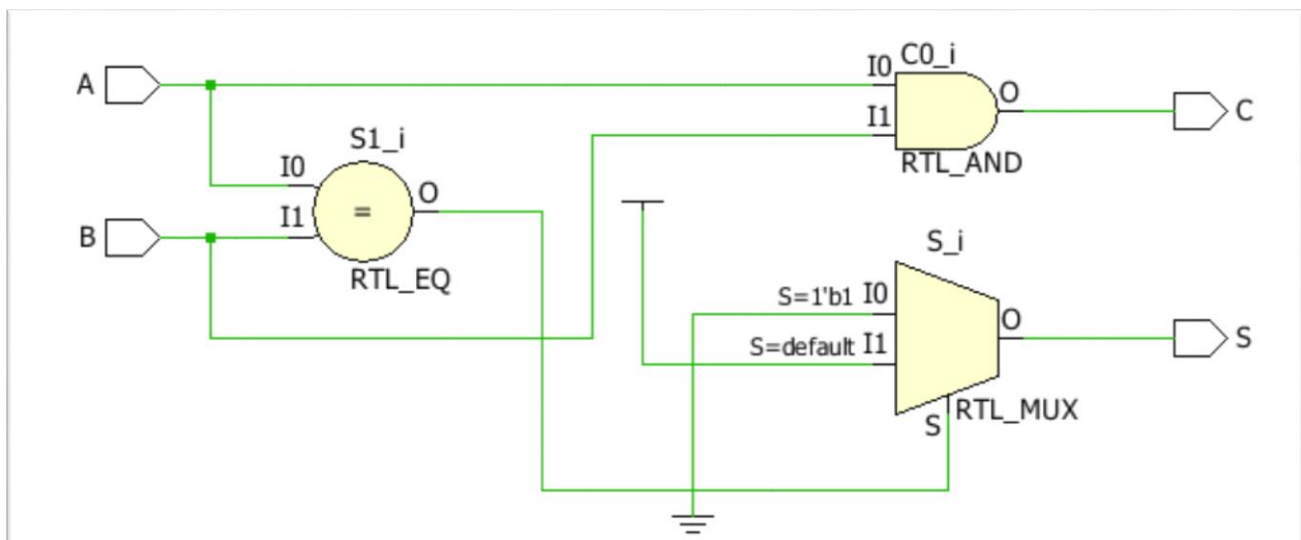

TBW Code

```

entity half_adder_gate_flow is

-- Port ( );

```

```
end half_adder_gate_flow;
```

architecture Behavioral of half_adder_gate_flow is

component HALF_ADDER is

```
Port( A: in STD_LOGIC;
```

```
      B: in STD_LOGIC;
```

```
      S: out STD_LOGIC;
```

```
      C: out STD_LOGIC);
```

```
end component;
```

```
Signal A1:STD_LOGIC:= '0';
```

```
Signal B1:STD_LOGIC:= '0';
```

```
Signal S1:STD_LOGIC;
```

```
Signal C1:STD_LOGIC;
```

```
begin
```

```
UUT:HALF_ADDER port map(A=>A1, B=>B1, S=>S1, C=>C1);
```

```
Stim_proc:process
```

```
begin
```

```
wait for 100ns;
```

```
A1<='0';B1<='0';
```

```
wait for 100ns;
```

```
A1<='0';B1<='1';
```

```
wait for 100ns;
```

```
A1<='1';B1<='0';
```

```
wait for 100ns;
```


```
A1<='1';B1<='1';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

TBW Waveform

 

FULL ADDER DATAFLOW MODEL

VHD code

entity FULL_ADDER is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : in STD_LOGIC;

S : out STD_LOGIC;

Cout : out STD_LOGIC);

end FULL_ADDER;

architecture DATAFLOW of FULL_ADDER is


begin

S<= (A XOR B) XOR C;

Cout<= (A AND B) OR (C AND B) OR (A AND C);

end DATAFLOW;

SCHEMEATIC DIAGRAM

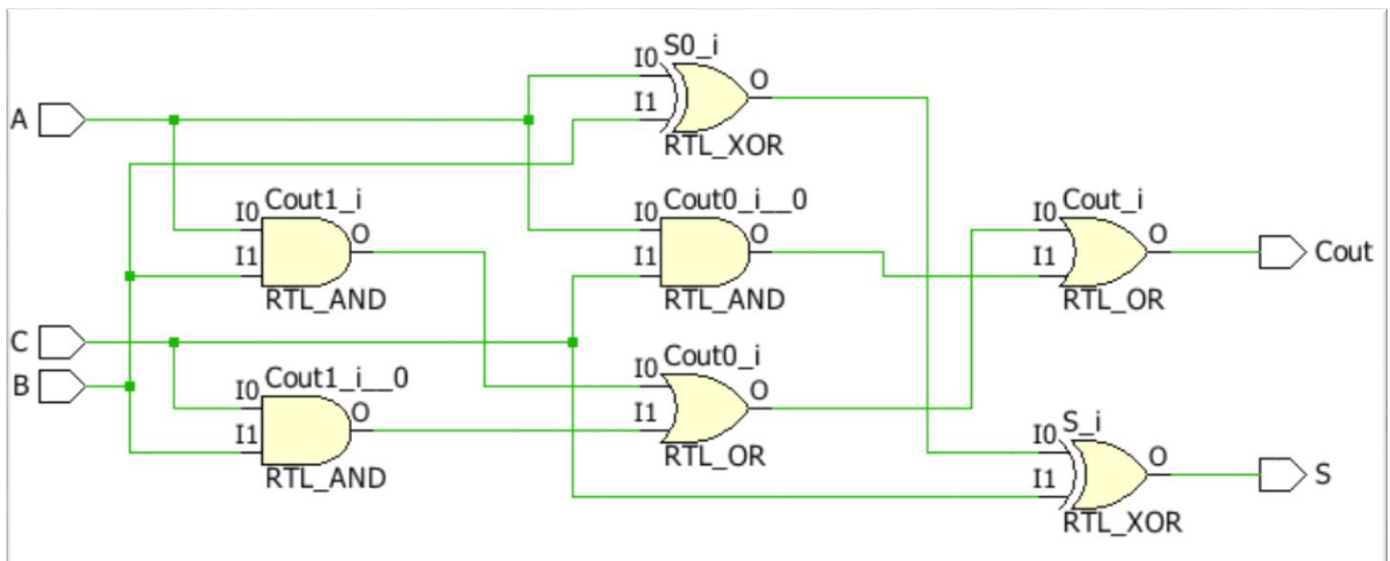

TBW Code

entity full_adder_gate_flow is

-- Port ();

end full_adder_gate_flow;

architecture DATAFLOW of full_adder_gate_flow is

component FULL_ADDER is

```
Port( A: in STD_LOGIC;
      B: in STD_LOGIC;
      C: in STD_LOGIC;
      S: out STD_LOGIC;
      Cout: out STD_LOGIC);
```

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC:= '0';

Signal S1:STD_LOGIC;

Signal Cout1:STD_LOGIC;

begin

UUT:FULL_ADDER port map(A=>A1, B=>B1, S=>S1, C=>C1, Cout=> Cout1);

Stim_proc:process

begin

wait for 100ns;

C1<='0';A1<='0';B1<='0';

wait for 100ns;

C1<='0';A1<='0';B1<='1';

wait for 100ns;

C1<='0';A1<='1';B1<='0';

wait for 100ns;

C1<='0';A1<='1';B1<='1';

wait for 100ns;

C1<='1';A1<='0';B1<='0';

wait for 100ns;

C1<='1';A1<='0';B1<='1';

wait for 100ns;

C1<='1';A1<='1';B1<='0';

wait for 100ns;


C1<='1';A1<='1';B1<='1';

wait;

```
end process;

end DATAFLOW;
```

TBW Waveform

 

FULL ADDER BEHAVIORAL MODEL

VHD code

```
entity FULL_ADDER is
    Port ( A : in STD_LOGIC;
           B : in STD_LOGIC;
           C : in STD_LOGIC;
           S : out STD_LOGIC;
           Cout : out STD_LOGIC);
end FULL_ADDER;

architecture Behavioral of FULL_ADDER is
begin
    process(A,B,C)
    begin
        if(A='0')then
            if(B=C)then
                S<='0';
            else
                S<='1';
            end if;
        else
            if(B=C)then
                S<='1';
            else
                S<='0';
            end if;
        end if;
    end process;
end architecture;
```

```

end if;

if(A='0')then

    if(B='1' and C='1')then

        Cout<='1';

    else

        Cout<='0';

    end if;

else

    if(B='0' and C='0')then

        Cout<='0';

    else

        Cout<='1';

    end if;


end if;

end process;

end Behavioral;

```

SCHEMEATIC DIAGRAM

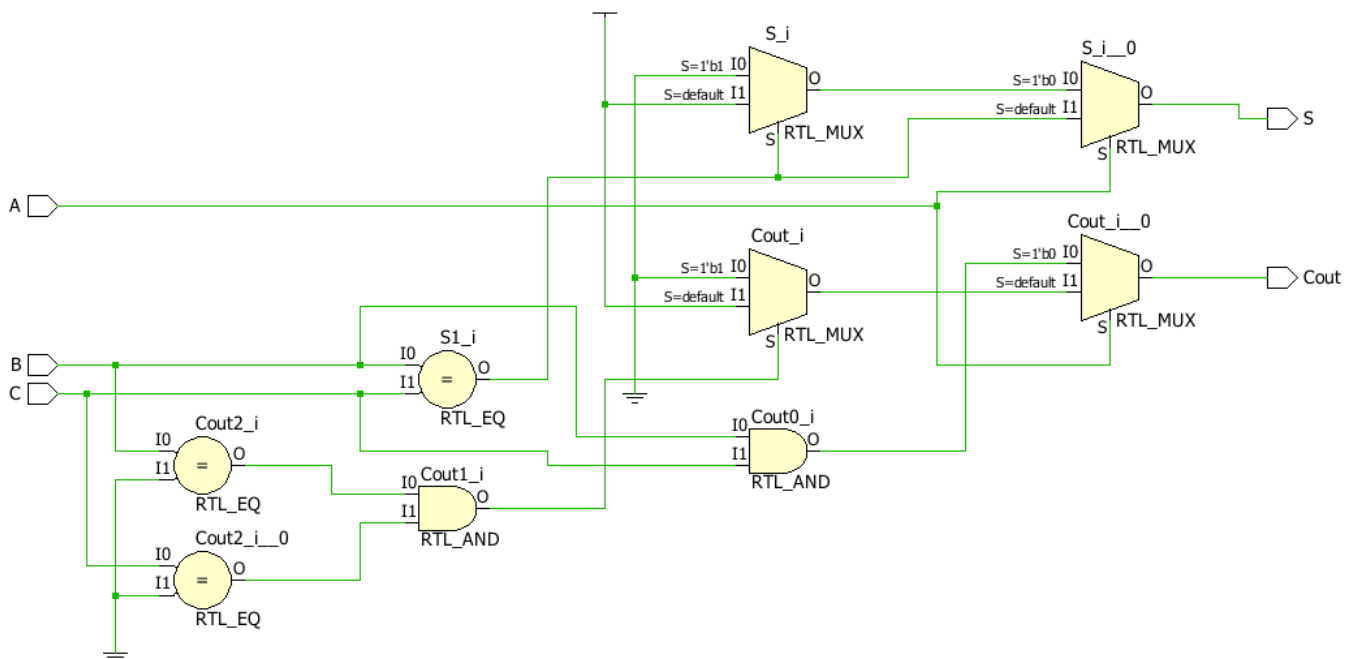

TBW Code

```

entity full_adder_gate_flow is

-- Port ();

end full_adder_gate_flow;

```

architecture Behavioral of full_adder_gate_flow is

component FULL_ADDER is

Port(A: in STD_LOGIC;

B: in STD_LOGIC;

C: in STD_LOGIC;

S: out STD_LOGIC;

Cout: out STD_LOGIC);

end component;

Signal A1:STD_LOGIC:= '0';

Signal B1:STD_LOGIC:= '0';

Signal C1:STD_LOGIC:= '0';

Signal S1:STD_LOGIC;

Signal Cout1:STD_LOGIC;

begin

UUT:FULL_ADDER port map(A=>A1, B=>B1, S=>S1, C=>C1, Cout=> Cout1);

Stim_proc:process

begin

wait for 100ns;

C1<='0';A1<='0';B1<='0';

wait for 100ns;

C1<='0';A1<='0';B1<='1';

wait for 100ns;

C1<='0';A1<='1';B1<='0';

wait for 100ns;

C1<='0';A1<='1';B1<='1';

wait for 100ns;

C1<='1';A1<='0';B1<='0';

wait for 100ns;

C1<='1';A1<='0';B1<='1';

wait for 100ns;

C1<='1';A1<='1';B1<='0';


wait for 100ns;

C1<='1';A1<='1';B1<='1';

wait;

```
end process;  
  
end Behavioral;
```

TBW Waveform

 

2:1 MUX DATAFLOW MODEL

VHD code

entity MUX is

Port (I0 : in STD_LOGIC;

I1 : in STD_LOGIC;

S : in STD_LOGIC;

O : out STD_LOGIC);

end MUX;


architecture DATAFLOW of MUX is

begin

O<=((NOT S)AND I0)OR (S AND I1);

end DATAFLOW;

SCHEMEATIC DIAGRAM

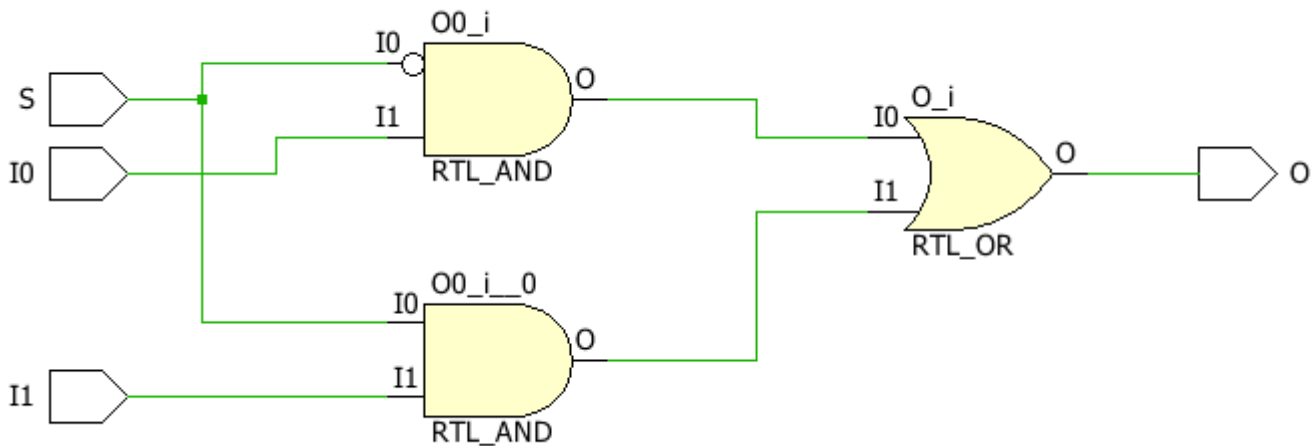

TBW Code

entity mux_gate_flow is

-- Port ();

end mux_gate_flow;

architecture DATAFLOW of mux_gate_flow is

component MUX is

Port(I0: in STD_LOGIC;

I1: in STD_LOGIC;

S: in STD_LOGIC;

O: out STD_LOGIC);

```

end component;

Signal I01:STD_LOGIC:= '0';

Signal I11:STD_LOGIC:= '1';

Signal S1:STD_LOGIC:= '0';

Signal O1:STD_LOGIC;

begin

UUT: MUX port map(I0=>I01,I1=>I11,S=>S1,O=>O1);

stim_proc: process

begin

wait for 100ns;

S1<='1';


wait;

end process;

end DATAFLOW;

```

TBW Waveform

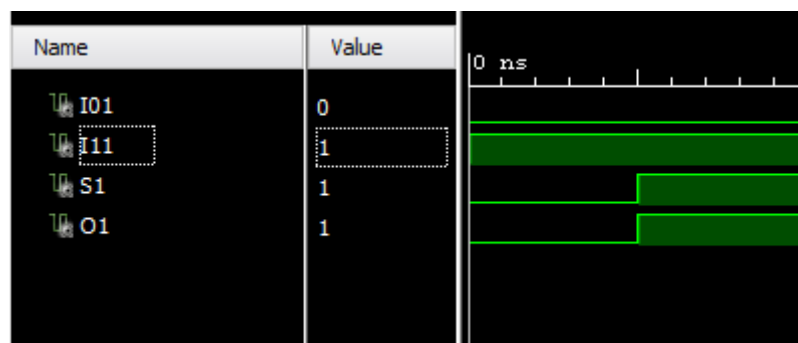

2:1 MUX BEHAVIORAL MODEL

VHD code

```

entity MUX is

Port ( S : in STD_LOGIC;

      I0 : in STD_LOGIC;

      I1 : in STD_LOGIC;

      O : out STD_LOGIC);

end MUX;

architecture Behavioral of MUX is

begin

process (S,I0,I1)

begin

```

```

if(S='0')then
O<=I0;

else
O<=I1;


end if;

end process;

end Behavioral;

```

SCHEMEATIC DIAGRAM

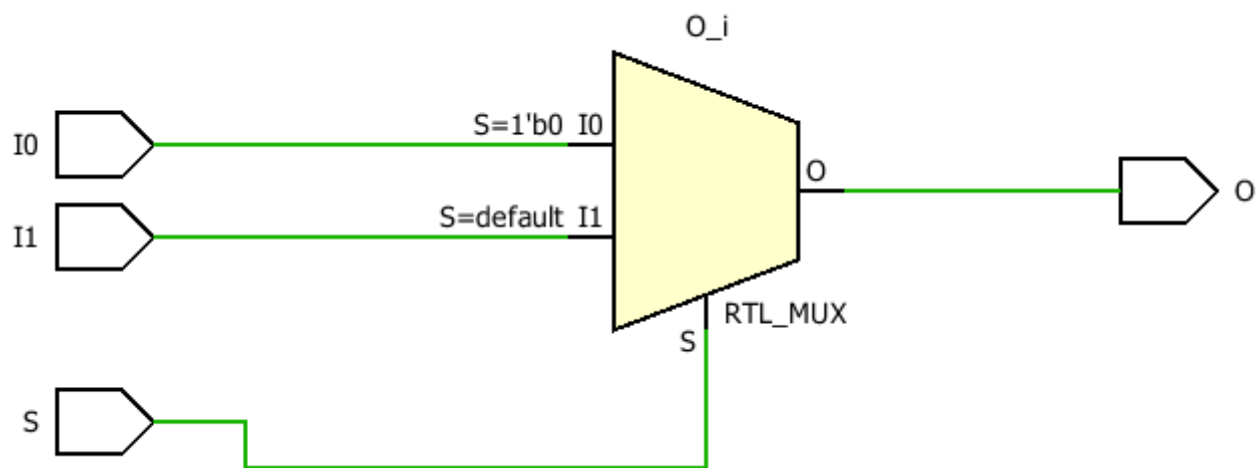

TBW Code

```

entity mux_gate_flow is
-- Port ( );
end mux_gate_flow;

architecture Behavioral of mux_gate_flow is

component MUX is
Port( I0: in STD_LOGIC;
      I1: in STD_LOGIC;
      S: in STD_LOGIC;
      O: out STD_LOGIC);
end component;

Signal I01:STD_LOGIC:= '0';
Signal I11:STD_LOGIC:= '1';
Signal S1:STD_LOGIC:= '0';
Signal O1:STD_LOGIC;

begin

```



```
UUT: MUX port map(I0=>I01,I1=>I11,S=>S1,O=>O1);
```

```
stim_proc: process
```

```
begin
```

```
wait for 100ns;
```


```
S1<='1';
```

```
wait;
```

```
end process;
```

```
end Behavioral;
```

TBW Waveform

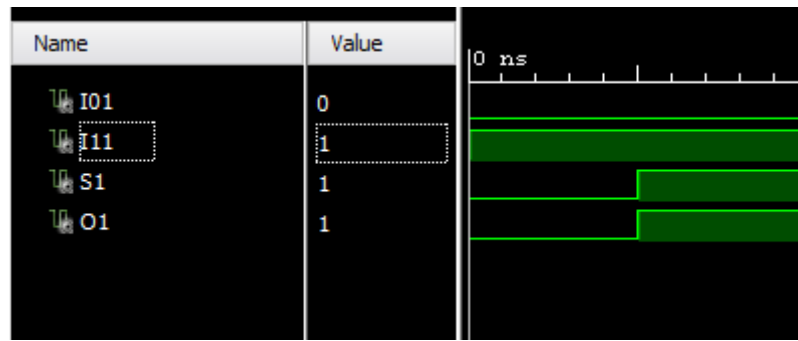

4:1 MUX DATAFLOW MODEL

VHD code

```
entity MUX is
```

```
Port ( I : in STD_LOGIC_VECTOR (3 downto 0);
```

```
      S : in STD_LOGIC_VECTOR (1 downto 0);
```

```
      O : out STD_LOGIC);
```

```
end MUX;
```

```
architecture DATAFLOW of MUX is
```

```
begin
```

```
O<=I(0) when S="00"else
```


```
  I(1) when S="01"else
```

```
  I(2) when S="10"else
```

```
  I(3);
```

```
end DATAFLOW;
```

SCHEMEATIC DIAGRAM

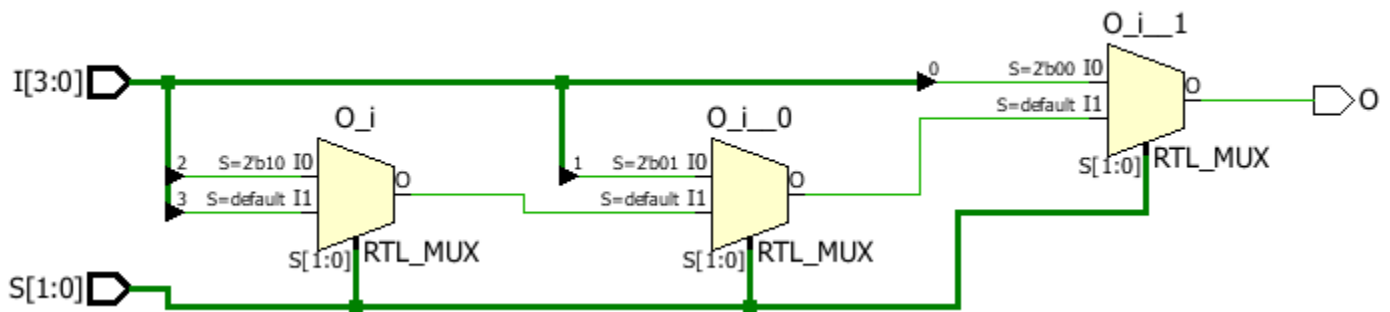

TBW Code

entity mux_gate_flow is

-- Port ();

end mux_gate_flow;

architecture DATAFLOW of mux_gate_flow is

component MUX is

Port (I : in STD_LOGIC_VECTOR (3 downto 0);

S : in STD_LOGIC_VECTOR (1 downto 0);

O : out STD_LOGIC);

end component;

signal I1: STD_LOGIC_VECTOR(3 downto 0):="0010";

signal S1: STD_LOGIC_VECTOR(1 downto 0):="00";

signal O1: STD_LOGIC;

begin

uut: MUX port map(I=>I1,S=>S1,O=>O1);

stim_proc: process

begin

wait for 100ns;

S1<="01";

wait for 100ns;

S1<="10";


wait for 100ns;

S1<="11";

end process;

end DATAFLOW;

TBW Waveform

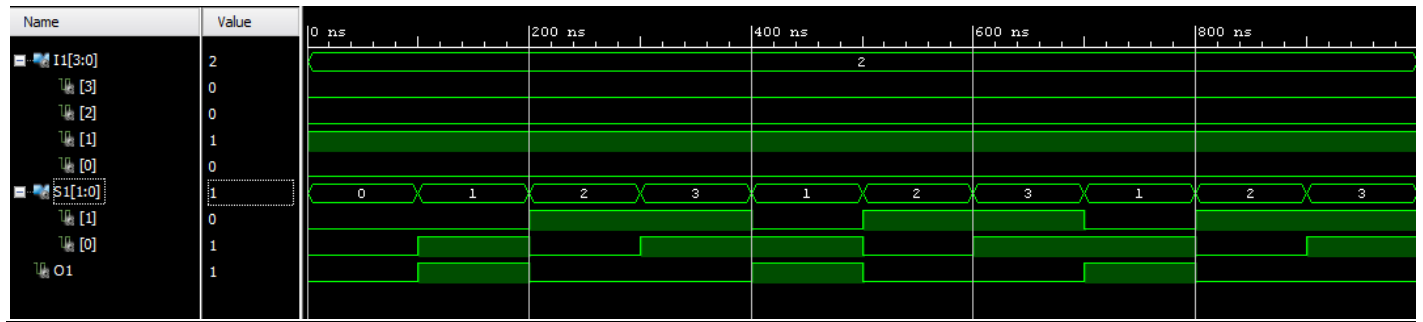

4:1 MUX BEHAVIORAL MODEL

VHD code

entity MUX is

Port (I : in STD_LOGIC_VECTOR (3 downto 0);

S : in STD_LOGIC_VECTOR (1 downto 0);

O : out STD_LOGIC);

end MUX;

architecture Behavioral of MUX is

begin

process(I,S)

begin

case S is

when "00"=>O<=I(0);

when "01"=>O<=I(1);

when "10"=>O<=I(2);

when "11"=>O<=I(3);


when others=>NULL;

end case;

end process;

end Behavioral;

SCHEMEATIC DIAGRAM

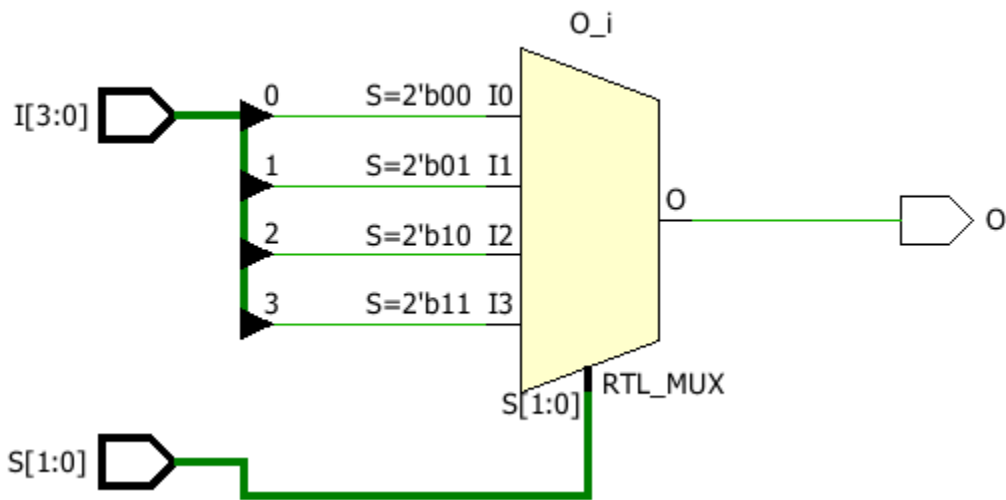

TBW Code

entity mux_gate_flow is

-- Port ();

end mux_gate_flow;

architecture Behavioral of mux_gate_flow is

component MUX is

Port (I : in STD_LOGIC_VECTOR (3 downto 0);

S : in STD_LOGIC_VECTOR (1 downto 0);

O : out STD_LOGIC);

end component;

signal I1: STD_LOGIC_VECTOR(3 downto 0):="0010";

signal S1: STD_LOGIC_VECTOR(1 downto 0):="00";

signal O1: STD_LOGIC;

begin

uut: MUX port map(I=>I1,S=>S1,O=>O1);

stim_proc: process

begin

wait for 100ns;

S1<="01";

wait for 100ns;

S1<="10";


wait for 100ns;

S1<="11";

```
end process;

end Behavioral;
```

TBW Waveform

 

3:8 DECODER BEHAVIORAL MODEL

VHD code

entity DECODE is

Port (I : in STD_LOGIC_VECTOR (2 downto 0);

O : out STD_LOGIC_VECTOR (7 downto 0));

end DECODE;

architecture Behavioral of DECODE is

begin

process(I)

begin

O<="00000000";

case I is

when "000"=> O(0) <='1';

when "001"=> O(1) <='1';

when "010"=> O(2) <='1';

when "011"=> O(3) <='1';

when "100"=> O(4) <='1';

when "101"=> O(5) <='1';

when "110"=> O(6) <='1';

when "111"=> O(7) <='1';


when others=>NULL;

end case;

end process;

end Behavioral;

SCHEMEATIC DIAGRAM

 

TBW Code

entity decode_gate_flow is

-- Port ();

end decode_gate_flow;

architecture Behavioral of decode_gate_flow is

component DECODE is

Port (I : in STD_LOGIC_VECTOR (2 downto 0);

O : out STD_LOGIC_VECTOR (7 downto 0));

end component;

signal I1: STD_LOGIC_VECTOR(2 downto 0):="000";

signal O1: STD_LOGIC_VECTOR(7 downto 0):="00000000";

begin

uut: DECODE port map(I=>I1,O=>O1);

stim_proc: process

begin

wait for 100ns;

I1<="001";

wait for 100ns;

I1<="010";

wait for 100ns;

I1<="011";

wait for 100ns;

I1<="100";

wait for 100ns;

```

I1<="101";

wait for 100ns;

I1<="110";

wait for 100ns;


I1<="111";

end process;

end Behavioral;

```

TBW Waveform

 

3:8 DECODER DATAFLOW MODEL

VHD code

entity DECODE is

Port (I : in STD_LOGIC_VECTOR (2 downto 0);

O : out STD_LOGIC_VECTOR (7 downto 0));

end DECODE;

architecture DATAFLOW of DECODE is

begin

O(0)<= '1' WHEN I="000" ELSE '0';

O(1)<= '1' WHEN I="001" ELSE '0';

O(2)<= '1' WHEN I="010" ELSE '0';

O(3)<= '1' WHEN I="011" ELSE '0';

O(4)<= '1' WHEN I="100" ELSE '0';


O(5)<= '1' WHEN I="101" ELSE '0';

O(6)<= '1' WHEN I="110" ELSE '0';

O(7)<= '1' WHEN I="111" ELSE '0';

end DATAFLOW;

SCHEMEATIC DIAGRAM

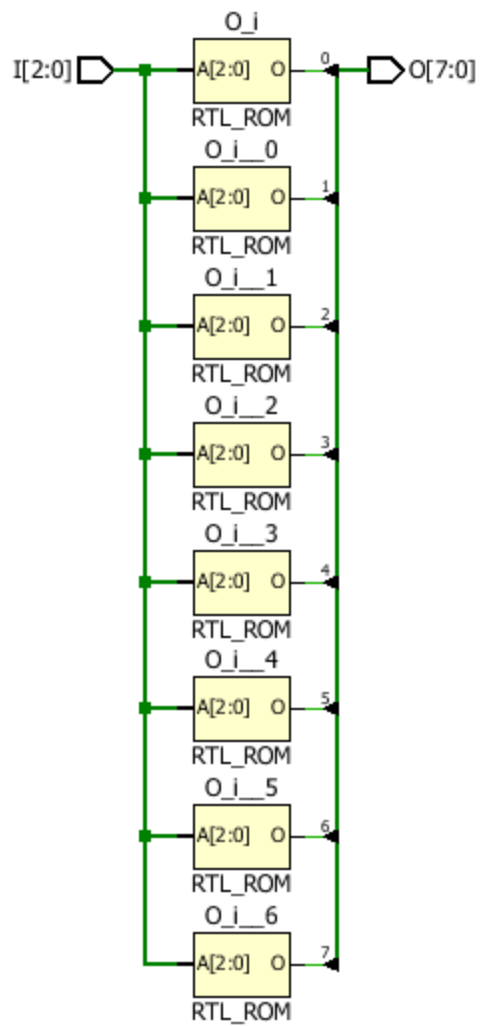

TBW Code

entity decode_gate_flow is

-- Port ();

end decode_gate_flow;

architecture DATAFLOW of decode_gate_flow is

component DECODE is

Port (I : in STD_LOGIC_VECTOR (2 downto 0);

O : out STD_LOGIC_VECTOR (7 downto 0));

end component;

signal I1: STD_LOGIC_VECTOR(2 downto 0):="000";

signal O1: STD_LOGIC_VECTOR(7 downto 0):="00000000";

begin

uut: DECODE port map(I=>I1,O=>O1);


```
stim_proc: process
```

```
begin
```

```
wait for 100ns;
```

```
l1<="001";
```

```
wait for 100ns;
```

```
l1<="010";
```

```
wait for 100ns;
```

```
l1<="011";
```

```
wait for 100ns;
```

```
l1<="100";
```

```
wait for 100ns;
```

```
l1<="101";
```

```
wait for 100ns;
```

```
l1<="110";
```


```
wait for 100ns;
```

```
l1<="111";
```

```
end process;
```

```
end DATAFLOW;
```

TBW Waveform

 

FULL ADDER (STRUCTURAL MODEL)

VHD code

```
entity FULL_ADDER_STR is
    Port ( X : in STD_LOGIC;
           Y : in STD_LOGIC;
           Z : in STD_LOGIC;
           Sum : out STD_LOGIC;
           Carry : out STD_LOGIC);
end FULL_ADDER_STR;

architecture STRUCTURAL of FULL_ADDER_STR is
    component HALF_ADDER is
        Port ( A : in STD_LOGIC;
              B : in STD_LOGIC;
              S : out STD_LOGIC;
              C : out STD_LOGIC);
    end component;


    component OR_GATE is
        Port ( A : in STD_LOGIC;
              B : in STD_LOGIC;
              C : out STD_LOGIC);
    end component;

    signal S1:STD_LOGIC;
    signal C1:STD_LOGIC;
    signal C2:STD_LOGIC;

    begin
        L1: HALF_ADDER port map(X,Y,S1,C1);
        L2: HALF_ADDER port map(S1,Z,Sum,C2);
        L3: OR_GATE port map(C1,C2,Carry);

    end STRUCTURAL;
```

SCHEMEATIC DIAGRAM

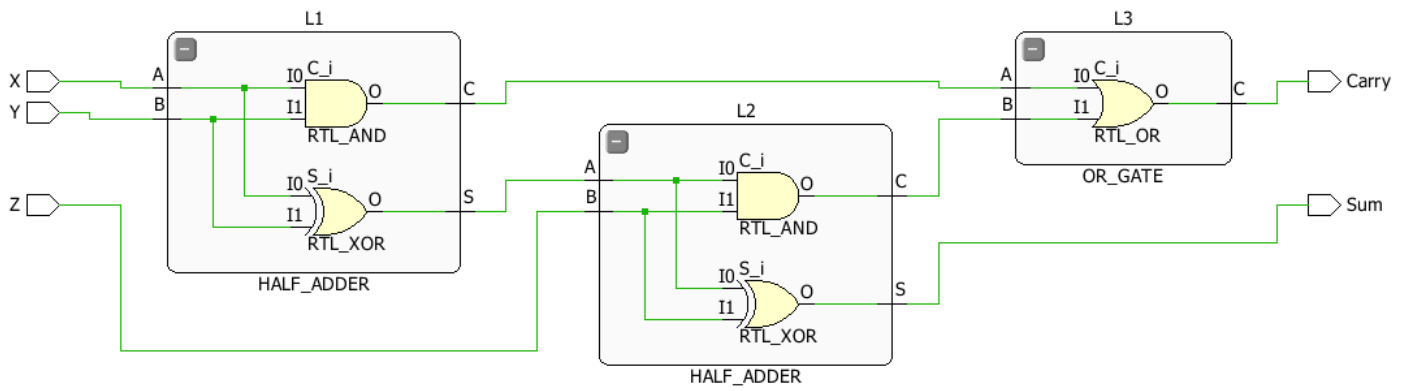

TBW Code

entity FULL_ADDER is

-- Port ();

end FULL_ADDER;

architecture STRUCTURAL of FULL_ADDER is

component FULL_ADDER_STR is

Port (X : in STD_LOGIC;

Y : in STD_LOGIC;

Z : in STD_LOGIC;

Sum : out STD_LOGIC;

Carry : out STD_LOGIC);

end component;

signal A1:STD_LOGIC:= '0';

signal B1:STD_LOGIC:= '0';

signal C1:STD_LOGIC:= '0';

signal S1:STD_LOGIC;

signal CY1:STD_LOGIC;

begin

uut: FULL_ADDER_STR Port Map(X=>A1,Y=>B1,Z=>C1,Sum=>S1,Carry=>CY1);

stim_proc:process

begin

A1<='0';


B1<='0';

C1<='0';

wait for 100ns;

```
A1<='0';  
B1<='0';  
C1<='1';  
wait for 100ns;  
A1<='0';  
B1<='1';  
C1<='0';  
wait for 100ns;  
A1<='0';  
B1<='1';  
C1<='1';  
wait for 100ns;  
A1<='1';  
B1<='0';  
C1<='0';  
wait for 100ns;  
A1<='1';  
B1<='0';  
C1<='1';  
wait for 100ns;  
A1<='1';  
B1<='1';  
C1<='0';  
wait for 100ns;  
A1<='1';  
B1<='1';  
C1<='1';  
wait;  
end process;  
end STRUCTURAL;
```

TBW Waveform

 

HALF ADDER (STRUCTURAL MODEL)

VHD code

entity HALF_ADDER_STR is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

S : out STD_LOGIC;

C : out STD_LOGIC);

end HALF_ADDER_STR;

architecture STRUCTURAL of HALF_ADDER_STR is

component XOR_GATE is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end component;

component AND_GATE is

Port (A : in STD_LOGIC;

B : in STD_LOGIC;

C : out STD_LOGIC);

end component;


begin

L1: AND_GATE port map(A,B,C);

L2: XOR_GATE port map(A,B,S);

end STRUCTURAL;

SCHEMEATIC DIAGRAM

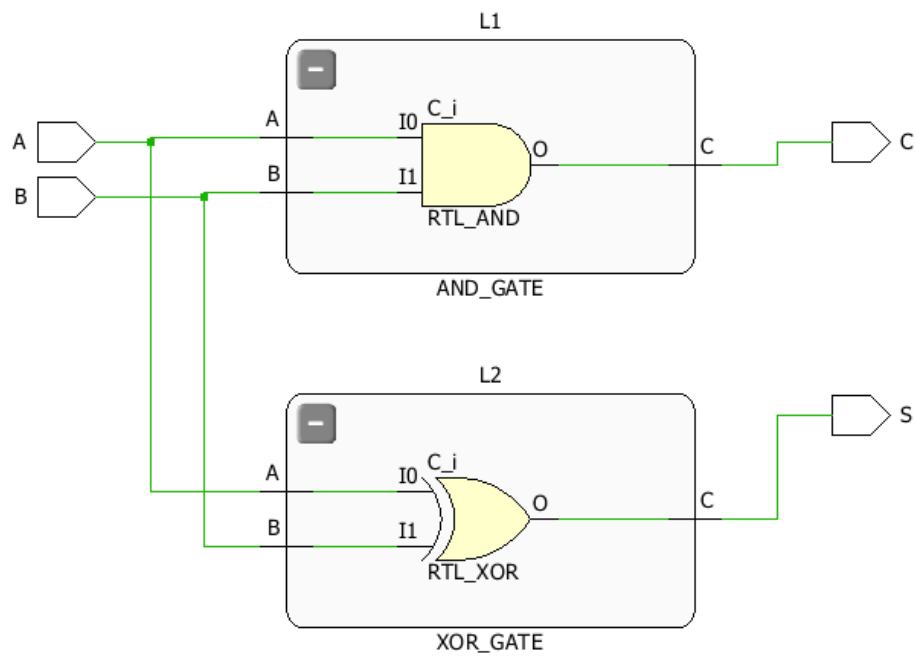

TBW Code

```

entity half_adder_str is
-- Port ( );
end half_adder_str;

architecture STRUCTURAL of half_adder_str is
component HALF_ADDER_STR is
    Port( A: in STD_LOGIC;
          B: in STD_LOGIC;
          S: out STD_LOGIC;
          C: out STD_LOGIC);
end component;

Signal A1:STD_LOGIC:= '0';
Signal B1:STD_LOGIC:= '0';
Signal S1:STD_LOGIC;
Signal C1:STD_LOGIC;

begin

uut: HALF_ADDER_STR Port Map(A=>A1,B=>B1,S=>S1,C=>C1);

Stim_proc:process
begin
wait for 100ns;

```

```

A1<='0';B1<='0';

wait for 100ns;

A1<='0';B1<='1';

wait for 100ns;

A1<='1';B1<='0';

wait for 100ns;

A1<='1';B1<='1';

wait;

end process;

end STRUCTURAL;

```

TBW Waveform

